Device Information

ISL98603

- 5 Channel DC/DC Converter + V_{ON} Slice + Power-Good
- Features Description
- iSim Design Simulation
 Tools And Support

Related Devices

- Technical Documentation
 Driving / Semples
- Pricing / Samples

Datasheet



ISL98603

5 Channel DC/DC Converter + V_{ON} Slice + Power-Good

Input Voltage (V)	9.5 to 15
V _{BOOST} (V)	10.83 to 19
Boost Current Limit (A)	5
V _{ON} (V)	up to 36
V _{OFF} (V)	down to -10
VLOGIC (V)	(Vlogic1) 2.5 to 3.3 (Vlogic2) 0.9 to 2.0
# of V _{COM}	N/A
# of Gamma	N/A
Features	Automatic Start-Up Sequencing, fault protection
Input Voltage (min) (V)	9.5
Input Voltage (max) (V)	15
V _{BOOST} (min) (V)	10.83
V _{BOOST} (max) (V)	19
V _{ON} (max) (V)	36
V _{OFF} (min) (V)	-10
V _{LOGIC} (min) (V)	2.5, 0.9
V _{LOGIC} (max) (V)	3.3, 2

Product Information

Key Features

9.5V to 15.0V Input Supply 1.3MHz Switching Frequency 5.0A Integrated Boost for Up to 19V A_{VDD} V_{ON} Charge Pump, Up to 36V and 120mA V_{OFF} Charge Pump, Down to -10V and 120mA Synchronous Buck1 for 3.3V/2.5V with 2.0A Peak FET Synchronous Buck2 Controller Output from 0.9V to 2.0V AVDD Delay Switch Capable of Soft-starting into a Highly Capacitive, Heavy Load V_{ON} Slice Function Integrated Power-Good Function for TCON Enable Automatic Start-Up Sequencing UVLO, UVP, OVP, OCP, and OTP Protection 40 Ld 6x6 QFN Specified for Ambient Operation Over the -40°C to +85°C Temperature Range Pb- Free (RoHS Compliant)

Description

The ISL98603 represents a high power, integrated LCD supply IC targeted at large panel LCD displays. The ISL98603 integrates a high power boost converter for AVDD generation, V_{ON} and V_{OFF} charge pump drivers, one synchronous buck regulator, and one synchronous buck controller for 2 logic voltages. The V_{ON} slicing circuitry and power-good function are also included.

Operating at 1.3MHz, the AVDD boost converter features a 5.0A boost FET. Feedback is taken from the far side of the delay FET for improving regulation. The OVP circuit protects output side components.

The logic synchronous buck converter features two 2.3A FETs operating at 1.3MHz internal clock. The output voltage is set by the IC internally or feedback resistor. The soft-start circuitry are also integrated with the buck.

The second logic voltage is generated from synchronous buck converter with MOSFET controllers. The overcurrent protection is also integrated with the buck.

The charge pump of V_{ON} and V_{OFF} use the full switching frequency and integrates the driver for high current capability. V_{ON} is further processed through an integrated V_{ON} Slice circuit in order to reduce flicker.

Alternative fixed voltages at the boost, Buck1, Buck2, V_{ON} charge pump, and V_{OFF} charge pump are available in ISL98603, please contact Intersil Marketing via email at rmonteir@intersil.com.

Packaging / Samples / Ordering

iBuy direct from Intersil Check distributor inventory	iBuy direct - out of P Available in RoHS/PI	· · · · · · · · · · · · · · · · · · ·	Request samples		
Part No.	Design-In Status	Temp.	Package	MSL	Թ
ISL98603IRAAZ	Active	Ind	40 Ld QFN	3	
ISL98603IRAAZ-T	Active	Ind	40 Ld QFN T+R	3	V 🥏
ISL98603IRAAZ-T7A	Active	Ind	40 Ld QFN T+R	3	
ISL98603IRAAZ-TK	Active	Ind	40 Ld QFN T+R	3	

MSL = Moisture Sensitivity Level - per IPC/JEDEC J-STD-020 **SMD** = Standard Microcircuit Drawing

Technical Documentation

Datasheet(s):

EN 5 Channel DC/DC Converter + V_{ON} Slice + Power-Good

Technical Homepage: Display Products

Tools And Support

iSim Design Simulation No Models Available

Applications

LCD TV

Related Devices

EL7515	High Frequency PWM Step-Up Regulator
EL7520	4-Channel DC/DC Controller
EL7520A	4-Channel DC/DC Controller
EL7581	3-Channel DC/DC Converter
EL7583	3-Channel DC/DC Converter
EL7586	TFT-LCD Power Supply
EL7586A	TFT-LCD Power Supply
EL7640	TFT-LCD DC/DC with Integrated Amplifiers



EL7640A	TFT-LCD DC/DC with Integrated Amplifiers
EL7641	TFT-LCD DC/DC with Integrated Amplifiers
EL7641A	TFT-LCD DC/DC with Integrated Amplifiers
EL7642	TFT-LCD DC/DC with Integrated Amplifiers
EL7642A	TFT-LCD DC/DC with Integrated Amplifiers
ISL78010	Automotive Grade TFT-LCD Power Supply
ISL78020	Automotive Grade TFT-LCD DC/DC with Integrated Amplifiers
ISL78022	Automotive Grade TFT-LCD DC/DC with Integrated Amplifiers
ISL97516	600kHz/1.2MHz PWM Step-Up Regulator
ISL97519	1% Output Accuracy 600kHz/1.2MHz PWM Step-Up Regulator
ISL97519A	600kHz/1.2MHz PWM Step-Up Regulator
ISL97522	4-Channel TFT-LCD Supply
ISL97536	Monolithic 1A Step-Down Regulator with Low Quiescent Current
ISL97642	TFT-LCD DC/DC with Integrated Amplifiers
ISL97645	Boost + V _{ON} Slice + V _{COM}
ISL97645A	Boost + V _{ON} Slice + V _{COM} + Reset
ISL97646	Boost + LDO + V _{ON} Slice + V _{COM}
ISL97650	4-Channel Integrated LCD Supply
ISL97650B	4-Channel Integrated LCD Supply
ISL97651	4-Channel Integrated LCD Supply
ISL97652	4-Channel Integrated LCD Supply with Dual $V_{\mbox{COM}}$ Amplifiers
ISL97653A	5-Channel Integrated LCD Supply
ISL97656	640kHz/1.2MHz PWM Step-Up Regulator
ISL98012	1.8V Input PWM Step-Up Regulator
ISL98602	5 Channel DC/DC Converter + V _{ON} Slice + Power Good

About Us | Careers | Contact Us | Investors | Legal | Privacy | Site Map | Subscribe | Intranet

intersil

©2003-2011. Intersil Americas Inc. All rights reserved.